


Computer Assignment 2

RISC-V single cycle implementation

Full Name	Student ID
Kourosh Alinaghi	810101476
Arshia Motaghian	810101503

Datapath

The design of the datapath:

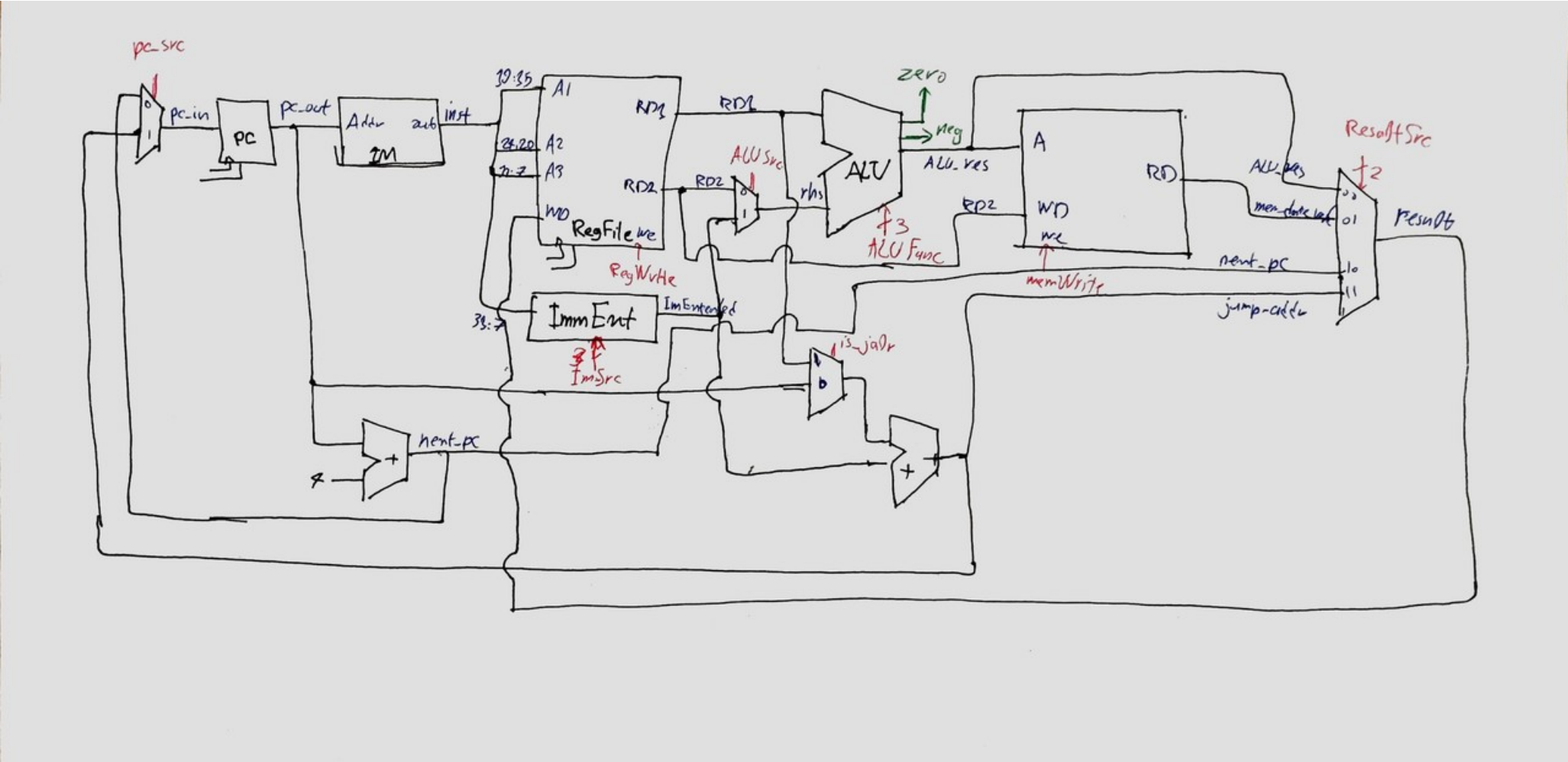

Controller

Controller has two modules:

Main Controller

This module issues all of the controlling signals that are directly used in datapath, except for `ALU_func` . It also has a `ALU_op` output which is used in ALU decoder to generate `ALU_func` .

Instruction type	PC_src	reg_write	ALU_src	mem_write	result_src	imm_src	ALU_op	is_jalr
Load word	0	1	1	0	01	I_TYPE	ADD_ANYWAY	0
Store word	0	0	1	1	00	S_TYPE	ADD_ANYWAY	0
Branch	depends on f3 , neg and zero	0	0	0	00	B_TYPE	SUB_ANYWAY	0
I-Type	0	1	1	0	00	I_TYPE	I_TYPE	0
Load upper immidiate	0	1	1	0	11	U_TYPE	I_TYPE	0
JAL	1	1	0	0	10	I_TYPE	ADD_ANYWAY	0
JALR	1	1	1	0	10	I_TYPE	ADD_ANYWAY	1

Branch PC_src

When the instruction type is `B_TYPE` , the value of `PC_src` is determines using `zero` and `neg` inputs from datapath like this:

Instruction	PC_src
beq	zero
bne	~zero
blt	neg
bqe	~neg or zero

ALU Decoder

This modules determines the value of `ALU_func` based on `ALU_op` , `f3` and `f7` inputs.

ALU_OP	f7	f3	ALU_func
ADD_ANYWAY	_	_	ADD_FUNC
SUB_ANYWAY	_	_	SUB_FUNC
R-TYPE	0000000	000	ADD_FUNC
R-TYPE	0100000	000	SUB_FUNC
R-TYPE	0000000	111	AND_FUNC
R-TYPE	0000000	110	OR_FUNC
R-TYPE	0000000	010	SLT_FUNC
R-TYPE	0000000	011	SLTU_FUNC
I-TYPE	_	000	ADD_FUNC
I-TYPE	_	100	XOR_FUNC
I-TYPE	_	110	OR_FUNC
I-TYPE	_	010	SLT_FUNC
I-TYPE	_	011	SLTU_FUNC